

Abstract: The purpose of this final project is to put together everything we have learned about digital logic from this course, and we get to choose our own project to demonstrate this fact.

Introduction: For this final project, I implemented the game Mastermind. This is a code breaking game that involves guessing a secret four-digit code, with each digit being a number in base four. The user inputs their guesses, and after each guess, the game will respond with hints. The user will know how many digits they guessed with the correct location and correct value, and how many digits they guessed with the correct value but wrong location. This lab requires many of the components used from previous labs, such as a LFSR for random code generation and finite state machines to input guesses.

Materials:

- Altera Terasic DE1-SoC Board with power and USB cables
- PC with Altera Quartus Prime Lite installed

Procedure: Mastermind

There are four major modules that control the functionality of the game. The first is a 5-bit LFSR to generate the random code. The flip flops in this module are slightly different from those in past labs in that when reset is true, the LFSR is enabled. Once reset is false, the LFSR is paused so that the code can be read from its random sequence. Each digit of the code is generated with two random bits from the LFSR.

The second module controls the inputs of the user's guesses and enables them to hit KEY3 to submit their guess. It is important to understand the difference between the current guess and the submitted guess. The current guess only depends on the state of the switches, which is a continuous and asynchronous input to the system. The submitted guess takes the current guess and saves it to be compared with the secret code. This module will make that distinction for us.

The third module is guess checker. It will first determine if each digit of our guess is in the correct location. If not, then it will determine if the digit exists, but in another location. Once all the digits have been compared, it will return to us how many digits of our guess are in the correct location, or just the correct value. The game is won when all four digits have been guessed in the correct locations.

The fourth module is a game mode selector. The user can choose to play a practice game, where they have unlimited guesses, or a real game, where they must find the correct code in 10 guesses.

There are also three major modules that control the displays for the game. The first is a state display that tells the user how many digits of their guess were in the correct location, and how many were just the correct value.

The second major display module is the guess counter. It tells the user how many guesses that have been made in the current game. In practice mode, the player gets unlimited guesses, so the counter will go from 0 to 99 before looping back to 0. In a real game, the counter only displays 0 to 9. If the player reaches their tenth guess and does not find the code, the display will read "loser."

The third major display module shows the current guesses. Once a game is over, regardless if the user is in practice mode or a real game, the displays will freeze to show the secret code.

There is an option to choose which set of information gets displays. The user can either have the status of the game be shown, which includes the accuracy of the guess and the number of guesses made. The other option is to have the current guess be displayed. The user can switch between these options at any time in during the game, and after a game is complete.

Results:

The overall game uses switches 9 through 0 and keys 3 through 1 as inputs. SW[9] is reset, SW[8] controls the display options, and SW[7:0] are used for the current guess inputs. KEY[3] is used to submit a guess, while KEY[2] is used to select practice mode and KEY[1] is used to select a real game. The user can switch between practice mode and a real game anytime during the game, but if they have exceeded 10 guesses in practice mode, switching to a real game will result in an immediate loss. A new game is set to practice mode by default. The hex displays are all used to show the desired information. On the status page, HEX4 shows the number of digits in the correct location, HEX2 shows the number of digits in the wrong location but correct value, and HEX1 and HEX0 count the total number of guesses. When a game is won, all inputs are locked except for the display toggle, and status display is frozen and the code is shown. On a loss, the only difference are that the status displays “loser” rather than the status of the game. The second option still displays the code. All major modules were tested using ModelSim and the total resource utilization is $(150 - 16) + (43 - 16) = 161$.

ModelSim Screenshots:

 


Figure 1: codeGenerator ModelSim screenshot

 


Figure 2: enterGuess ModelSim screenshot

 


Figure 3: comparator ModelSim screenshot

 


Figure 4: sum ModelSim screenshot

 


Figure 5: gameMode ModelSim screenshot

 


Figure 6: gameLimit ModelSim screenshot

 


Figure 7: stateDisplay ModelSim screenshot

 


Figure 8: counter ModelSim screenshot

System Cost:

Analysis & Synthesis Resource Utilization by Entity										
<<Filter>>										
Compilation Hierarchy Node	Combinational ALUTs	Dedicated Logic Registers	Block Memory Bits	DSP Blocks	Pins	Virtual Pins	Full Hierarchy Name	Entity Name	Library Name	
1 DE1_SoC	150 (60)	43 (0)	0	0	67	0	DE1_SoC	DE1_SoC	work	
1 clock_divider:cdv	16 (16)	16 (16)	0	0	0	0	DE1_SoC clock_divider:cdv	clock_divider	work	
2 codeGenerator:rmg	1 (1)	5 (5)	0	0	0	0	DE1_SoC codeGenerator:rmg	codeGenerator	work	
3 comparator:C0	4 (4)	0 (0)	0	0	0	0	DE1_SoC comparator:C0	comparator	work	
4 comparator:C1	2 (2)	0 (0)	0	0	0	0	DE1_SoC comparator:C1	comparator	work	
5 comparator:C2	3 (3)	0 (0)	0	0	0	0	DE1_SoC comparator:C2	comparator	work	
6 comparator:C3	4 (4)	0 (0)	0	0	0	0	DE1_SoC comparator:C3	comparator	work	
7 counter:guessesMade	31 (31)	16 (16)	0	0	0	0	DE1_SoC cou...guessesMade	counter	work	
8 enterGuess:guess	13 (13)	2 (2)	0	0	0	0	DE1_SoC enterGuess:guess	enterGuess	work	
9 gameLimit:rounds	4 (4)	0 (0)	0	0	0	0	DE1_SoC gameLimit:rounds	gameLimit	work	
10 gameMode:practice	3 (3)	2 (2)	0	0	0	0	DE1_SoC gameMode:practice	gameMode	work	
11 stateDisplay:CL	2 (2)	2 (2)	0	0	0	0	DE1_SoC stateDisplay:CL	stateDisplay	work	
12 stateDisplay:VO	2 (2)	0 (0)	0	0	0	0	DE1_SoC stateDisplay:VO	stateDisplay	work	
13 sum:totalCL	2 (2)	0 (0)	0	0	0	0	DE1_SoC sum:totalCL	sum	work	
14 sum:totalVO	1 (1)	0 (0)	0	0	0	0	DE1_SoC sum:totalVO	sum	work	
15 winCondition:win	2 (2)	0 (0)	0	0	0	0	DE1_SoC winCondition:win	winCondition	work	

Figure 9: Resource utilization by entity screenshot

Analysis and Conclusion:

Overall, the final project was an opportunity to combine important concepts of previous labs into one system. Previously topics from both combinational logic and sequential logic were needed to complete this project. There was also a new component learned in this project in that the end was not a completely static system. Rather than having everything frozen at the end, we have a variable display option to check how we did in the game we just completed.

Appendix:

```
module codeGenerator(clk, reset, code3, code2, code1, code0);
    input logic clk, reset;
    output reg [1:0] code3, code2, code1, code0;

    // State variables
    reg [4:0] ps = 5'b0000;
    reg [4:0] ns;
    reg in;

    // Next state logic
    always_comb begin
        in = ~(ps[4] ^ ps[2]);
        ns = {ps[3:0], in};
    end

    // Output logic
    assign code3 = {ps[4], ps[1]};
    assign code2 = {ps[2], ps[4]};
    assign code1 = {ps[0], ps[1]};
    assign code0 = {ps[1], ps[3]};

    // DFFs
    always_ff @(posedge clk) begin
        if (reset)
            ps <= ns;
        else
            ps <= ps;
    end
endmodule

module codeGenerator_tb();
    logic clk, reset;
    logic [1:0] code3, code2, code1, code0;

    codeGenerator dut(clk, reset, code3, code2, code1, code0);

    // Set up the clock.
    parameter CLOCK_PERIOD = 100;
    initial begin
        clk <= 0;
        forever #(CLOCK_PERIOD/2) clk <= ~clk;
    end

    // Set up initial inputs to the design. Each line is a clock cycle.
    integer i;
    initial begin
        reset <= 1; @(posedge clk);
        reset <= 0;
        for(i = 0; i < 10; i++) begin
            @(posedge clk);
        end
        reset <= 1;
        for(i = 0; i < 10; i++) begin
            @(posedge clk);
        end
        reset <= 0;
        for(i = 0; i < 10; i++) begin
            @(posedge clk);
        end
        reset <= 1;
        for(i = 0; i < 10; i++) begin
            @(posedge clk);
        end
        reset <= 0;
    end
endmodule
```

```

        for(i = 0; i < 10; i++) begin
            @(posedge clk);
        end
        reset <= 1;
        for(i = 0; i < 10; i++) begin
            @(posedge clk);
        end
        $stop; // End simulation
    end
endmodule

```

Code 1: codeGenerator.sv

```

module enterGuess(clk, reset, guess3, guess2, guess1, guess0, enter, out3, out2, out1, out0);
    input logic clk, reset, enter;
    input logic [1:0] guess3, guess2, guess1, guess0;
    output logic [1:0] out3, out2, out1, out0;

    // State variables
    enum {A, B, C} ps, ns;

    // Next state logic
    always_comb begin
        case (ps)
            A: if (enter)
                ns = B;
            else
                ns = A;
            B: if (enter)
                ns = C;
            else
                ns = A;
            C: if (enter)
                ns = C;
            else
                ns = A;
        endcase
    end

    // Output logic
    always @(*) begin
        if (ns == B) begin
            out3 = guess3;
            out2 = guess2;
            out1 = guess1;
            out0 = guess0;
        end
    end

    // DFFs
    always_ff @(posedge clk) begin
        if (reset)
            ps <= A;
        else
            ps <= ns;
        end
    end
endmodule

module enterGuess_tb();
    logic clk, reset, enter;
    logic [1:0] guess3, guess2, guess1, guess0, out3, out2, out1, out0;

    enterGuess dut(clk, reset, guess3, guess2, guess1, guess0, enter, out3, out2, out1, out0);

    // Set up the clock.
    parameter CLOCK_PERIOD = 100;
    initial begin
        clk <= 0;
        forever #(CLOCK_PERIOD/2) clk <= ~clk;
    end
end

```



```

// Set up initial inputs to the design. Each line is a clock cycle.
initial begin
    reset <= 1; @(posedge clk);
    reset <= 0; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b11; guess1 <= 2'b10; guess0 <= 2'b01; enter <= 1; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b11; guess1 <= 2'b10; guess0 <= 2'b01; enter <= 1; @(posedge clk);
    guess3 <= 2'b11; guess2 <= 2'b00; guess1 <= 2'b00; guess0 <= 2'b11; enter <= 0; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b01; guess1 <= 2'b10; guess0 <= 2'b11; enter <= 0; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b11; guess1 <= 2'b10; guess0 <= 2'b01; enter <= 0; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b01; guess1 <= 2'b10; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b11; guess1 <= 2'b10; guess0 <= 2'b01; enter <= 0; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b01; guess1 <= 2'b10; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b11; guess1 <= 2'b10; guess0 <= 2'b01; enter <= 0; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b01; guess1 <= 2'b10; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b01; guess2 <= 2'b01; guess1 <= 2'b11; guess0 <= 2'b11; enter <= 1; @(posedge clk);
    guess3 <= 2'b00; guess2 <= 2'b11; guess1 <= 2'b10; guess0 <= 2'b01; enter <= 0; @(posedge clk);
    $stop; // End simulation
end
endmodule

```

Code 2: enterGuess.sv

```

module comparator(reset, guess, codeA, codeB, codeC, codeD, correctLocation, valueOnly);
    input logic reset;
    input logic [1:0] guess, codeA, codeB, codeC, codeD;
    output logic [2:0] correctLocation, valueOnly;

    always @(*) begin
        if (reset) begin
            correctLocation = 3'b000;
            valueOnly = 3'b000;
        end else if (guess == codeA) begin
            correctLocation = 3'b001;
            valueOnly = 3'b000;
        end else begin
            if (guess == codeB)
                valueOnly = 3'b001;
            else if (guess == codeC)
                valueOnly = 3'b001;
            else if (guess == codeD)
                valueOnly = 3'b001;
            else begin
                valueOnly = 3'b000;
            end
            correctLocation = 3'b000;
        end
    end
end
endmodule

module comparator_tb();
    logic reset;
    logic [1:0] guess, codeA, codeB, codeC, codeD;
    logic [2:0] correctLocation, valueOnly;

    comparator dut(reset, guess, codeA, codeB, codeC, codeD, correctLocation, valueOnly);

    initial begin
        reset = 1; #10;
        reset = 0; #10;
        guess = 2'b00; codeA = 2'b00; codeB = 2'b11; codeC = 2'b10; codeD = 2'b10; #10;
        guess = 2'b00; codeA = 2'b11; codeB = 2'b11; codeC = 2'b10; codeD = 2'b00; #10;
        guess = 2'b00; codeA = 2'b11; codeB = 2'b11; codeC = 2'b00; codeD = 2'b10; #10;
        guess = 2'b00; codeA = 2'b11; codeB = 2'b11; codeC = 2'b10; codeD = 2'b10; #10;
    end
endmodule

```

Code 3: comparator.sv

```

module sum(value3, value2, value1, value0, sum);
    input logic [3:0] value3, value2, value1, value0;
    output logic [3:0] sum;

    assign sum = value3 + value2 + value1 + value0;
endmodule

module sum_tb();
    logic [3:0] value3, value2, value1, value0, sum;

    sum dut(value3, value2, value1, value0, sum);

    initial begin
        value3 = 3'b000; value2 = 3'b000; value1 = 3'b000; value0 = 3'b000; #10;
        value3 = 3'b000; value2 = 3'b000; value1 = 3'b000; value0 = 3'b001; #10;
        value3 = 3'b000; value2 = 3'b000; value1 = 3'b001; value0 = 3'b001; #10;
        value3 = 3'b000; value2 = 3'b001; value1 = 3'b001; value0 = 3'b001; #10;
        value3 = 3'b001; value2 = 3'b001; value1 = 3'b001; value0 = 3'b001; #10;
    end
endmodule

```

Code 4: sum.sv

```

module gameMode(clk, reset, on, off, gameOverL, gameOverw, realGame);
    input logic clk, reset, on, off, gameOverL, gameOverw;
    output logic realGame;

    // State variables
    enum {A, B, C, D} ps, ns;

    // Next state logic
    always_comb begin
        case (ps)
            A: if (gameOverL)
                ns = C;
                else if (gameOverw)
                ns = D;
                else if (on)
                ns = B;
                else
                ns = A;
            B: if (gameOverL)
                ns = C;
                else if (gameOverw)
                ns = C;
                else if (off)
                ns = A;
                else
                ns = B;
            C: ns = C;
            D: ns = D;
        endcase
    end

    // Output logic
    always_comb begin
        case (ps)
            A: realGame = 1'b0;
            B: realGame = 1'b1;
            C: realGame = 1'b1;
            D: realGame = 1'b0;
        endcase
    end
end

```

```

// DFFs
always_ff @(posedge clk) begin
    if (reset)
        ps <= A;
    else
        ps <= ns;
    end
endmodule

module gameMode_tb();
    logic clk, reset, on, off, gameOverL, gameOverW, realGame;

    gameMode dut(clk, reset, on, off, gameOverL, gameOverW, realGame);

    // Set up the clock.
    parameter CLOCK_PERIOD = 100;
    initial begin
        clk <= 0;
        forever #(CLOCK_PERIOD/2) clk <= ~clk;
    end

    // Set up initial inputs to the design. Each line is a clock cycle.
    initial begin
        reset <= 1;
        reset <= 0;
        on <= 1;
        on <= 0;
        off <= 1;
        off <= 0;
        gameOverL <= 1;
        gameOverL <= 0;
        gameOverW <= 1;
        gameOverW <= 0;

        $stop;
    end
endmodule

```

Code 5: gameMode.sv

```

module gameLimit(reset, totalGuesses, game, over);
    input logic reset, game;
    input logic [7:0] totalGuesses;
    output logic over;

    always @(*) begin
        if (game)
            if (totalGuesses > 8'b00001001)
                over = 1'b1;
            else
                over = 1'b0;
        else
            over = 1'b0;
        end
    end
endmodule

```



```

module gameLimit_tb();
    logic reset, game;
    logic [7:0] totalGuesses;
    logic over;

    gameLimit dut(reset, totalGuesses, game, over);

    integer i;
    initial begin
        reset = 1;   game = 1;   #10;
        reset = 0;   #10;
        for(i=0; i<20; i++) begin
            totalGuesses[7:0] = i; #10;
        end
    end
endmodule

```

Code 6: gameLimit.sv

```

module winCondition(correctLocation, win);
    input logic [2:0] correctLocation;
    output logic win;

    assign win = (correctLocation == 3'b100);
endmodule

```

Code 7: winCondition.sv

```

module stateDisplay(clk, reset, in, value, displayout);
    input logic clk, reset, in;
    input logic [2:0] value;
    output logic [6:0] displayout;

    // State variables
    enum {A, B, C, D} ps, ns;

    // Nest state logic
    always_comb begin
        case (ps)
            A: if (in)
                ns = C;
                else
                ns = A;
            B: if (in)
                ns = C;
                else
                ns = B;
            C: if (in)
                ns = D;
                else
                ns = B;
            D: if (in)
                ns = D;
                else
                ns = B;
        endcase
    end
endmodule

```

```

// output logic
always_comb begin
    case (ps)
        A: displayOut = 7'b1000000;
        default: case (value)
            3'b000: displayOut = 7'b1000000; // 0
            3'b001: displayOut = 7'b1111001; // 1
            3'b010: displayOut = 7'b0100100; // 2
            3'b011: displayOut = 7'b0110000; // 3
            3'b100: displayOut = 7'b0011001; // 4
            default: displayOut = 7'b1111111;
        endcase
    endcase
end

// DFFs
always_ff @(posedge clk) begin
    if (reset)
        ps <= A;
    else
        ps <= ns;
    end
endmodule

module stateDisplay_tb();
    logic clk, reset, in;
    logic [2:0] value;
    logic [6:0] displayOut;

    stateDisplay dut(clk, reset, in, value, displayOut);

    // Set up the clock.
    parameter CLOCK_PERIOD = 100;
    initial begin
        clk <= 0;
        forever #(CLOCK_PERIOD/2) clk <= ~clk;
    end

    // Set up initial inputs to the design. Each line is a clock cycle.
    integer i;
    initial begin
        reset <= 1; in <= 1; @(posedge clk);
        reset <= 0; in <= 0; @(posedge clk);
        for(i=0; i<5; i++) begin
            value <= i; @(posedge clk);
            @(posedge clk);
            @(posedge clk);
            in <= 1; @(posedge clk);
            in <= 0; @(posedge clk);
        end
        $stop;
    end
endmodule

```

Code 8: stateDisplay.sv

```

module counter(reset, in, displayOut10, displayOut1, guesses);
    input logic reset, in;
    output logic [6:0] displayOut10, displayOut1;
    output logic [7:0] guesses;

    reg [3:0] count1, count10;

    // Counters
    always @(posedge in or posedge reset) begin
        if (reset) begin
            count1 <= 4'b0000;
            count10 <= 4'b0000;
            guesses <= 0;
        end else if (in) begin
            guesses = guesses + 1;
            if (count1 < 9)
                count1 <= count1 + 4'b0001;
            else begin
                if (count10 < 9)
                    count10 <= count10 + 1;
                else
                    count10 <= 0;
                    count1 = 0;
            end
        end
    end

    // Ones place display
    always @(count1) begin
        case (count1)
            4'b0000: displayOut1 = 7'b1000000; // 0
            4'b0001: displayOut1 = 7'b1111001; // 1
            4'b0010: displayOut1 = 7'b0100100; // 2
            4'b0011: displayOut1 = 7'b0110000; // 3
            4'b0100: displayOut1 = 7'b0011001; // 4
            4'b0101: displayOut1 = 7'b0010010; // 5
            4'b0110: displayOut1 = 7'b0000010; // 6
            4'b0111: displayOut1 = 7'b1111000; // 7
            4'b1000: displayOut1 = 7'b0000000; // 8
            4'b1001: displayOut1 = 7'b0010000; // 9
            default: displayOut1 = 7'b1111111;
        endcase
    end

    // Tens place display
    always @(count10) begin
        case (count10)
            4'b0000: displayOut10 = 7'b1000000; // 0
            4'b0001: displayOut10 = 7'b1111001; // 1
            4'b0010: displayOut10 = 7'b0100100; // 2
            4'b0011: displayOut10 = 7'b0110000; // 3
            4'b0100: displayOut10 = 7'b0011001; // 4
            4'b0101: displayOut10 = 7'b0010010; // 5
            4'b0110: displayOut10 = 7'b0000010; // 6
            4'b0111: displayOut10 = 7'b1111000; // 7
            4'b1000: displayOut10 = 7'b0000000; // 8
            4'b1001: displayOut10 = 7'b0010000; // 9
            default: displayOut10 = 7'b1111111;
        endcase
    end
endmodule

```

```

module counter_tb();
  logic clk, reset, in;
  logic [6:0] displayOut10, displayOut1;
  logic [3:0] count1, count10;
  logic [7:0] guesses;

  counter dut(reset, in, displayOut10, displayOut1, guesses);

  // Set up the clock.
  parameter CLOCK_PERIOD = 100;
  initial begin
    clk <= 0;
    forever #(CLOCK_PERIOD/2) clk <= ~clk;
  end

  // Set up initial inputs to the design. Each line is a clock cycle.
  integer i;
  initial begin
    reset <= 1; in <= 0; @(posedge clk);
    reset <= 0;
    for(i=0; i<30; i++) begin
      in <= 1; @(posedge clk);
      in <= 0; @(posedge clk);
    end
    $stop;
  end
endmodule

```

Code 9: counter.sv

```

module guessDisplay(value, displayOut);
  input logic [1:0] value;
  output logic [6:0] displayOut;

  always_comb begin
    case (value)
      2'b00: displayOut = 7'b1000000; // 0
      2'b01: displayOut = 7'b1111001; // 1
      2'b10: displayOut = 7'b0100100; // 2
      2'b11: displayOut = 7'b0110000; // 3
    endcase
  end
endmodule

```

Code 10: guessDisplay.sv


```

module DE1_Soc (CLOCK_50, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, KEY, LEDR, SW);
input logic CLOCK_50; // 50MHz clock.
output logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
output logic [9:0] LEDR;
input logic [3:0] KEY; // True when not pressed, False when pressed
input logic [9:0] SW;

// Generate clk off of CLOCK_50, whichClock picks rate.
logic [31:0] clk;
parameter whichClock = 15;
clock_divider cddiv (CLOCK_50, clk);

// Hook up FSM inputs and outputs.
assign reset = SW[9]; // reset
assign enterGuess = ~KEY[3]; // push to submit current guess
assign LEDR[0] = wonGame; // true if won game
assign LEDR[9] = lostGame; // true if lost game
assign LEDR[7] = gameMode; // true if not practice game
logic [1:0] digit3, digit2, digit1, digit0; // four digit code
logic [1:0] guessD3, guessD2, guessD1, guessD0; // selected guesses
logic [7:0] totalGuesses; // number of guesses made
logic [3:0] CL3, CL2, CL1, CL0; // number of correct values and correct locations
logic [3:0] VO3, VO2, VO1, VO0; // number of correct values but wrong locations
logic [3:0] totalCorrect, totalValuesOnly; // total number of CL and VO
logic [6:0] guessDisp3, guessDisp2, guessDisp1, guessDisp0; // hex displays for guesses
logic [6:0] codeDisp3, codeDisp2, codeDisp1, codeDisp0; // hex displays for code
logic [6:0] locationDisp, valueDisp, counter10, counter1; // hex displays for game states

// Random code generator
codeGenerator rng(c.clk(clk[whichClock]), .reset, .code3(digit3), .code2(digit2), .code1(digit1), .code0(digit0));

// Make guess
enterGuess guess(c.clk(clk[whichClock]), .reset, .guess3({SW[7], SW[6]}), .guess2({SW[5], SW[4]}), .guess1({SW[3], SW[2]}), .guess0({SW[1], SW[0]}),
    .enter(enterGuess || wonGame || lostGame), .out3(guessD3), .out2(guessD2), .out1(guessD1), .out0(guessD0));

// Compare guess with code
comparator C3(.reset, .guess(guessD3), .codeA(digit3), .codeB(digit2), .codeC(digit1), .codeD(digit0), .correctLocation(CL3), .valueOnly(VO3));
comparator C2(.reset, .guess(guessD2), .codeA(digit2), .codeB(digit3), .codeC(digit1), .codeD(digit0), .correctLocation(CL2), .valueOnly(VO2));
comparator C1(.reset, .guess(guessD1), .codeA(digit1), .codeB(digit3), .codeC(digit2), .codeD(digit0), .correctLocation(CL1), .valueOnly(VO1));
comparator C0(.reset, .guess(guessD0), .codeA(digit0), .codeB(digit3), .codeC(digit2), .codeD(digit1), .correctLocation(CL0), .valueOnly(VO0));

// Finds total correct locations and total values only
sum totalCL(.value3(CL3), .value2(CL2), .value1(CL1), .value0(CL0), .sum(totalCorrect));
sum totalVO(.value3(VO3), .value2(VO2), .value1(VO1), .value0(VO0), .sum(totalValuesOnly));

// win condition
winCondition win(.correctLocation(totalCorrect), .win(wonGame));

// select game mode
gameMode practice(c.clk(clk[whichClock]), .reset, .on(~KEY[1]), .off(~KEY[2]), .gameOverL(lostGame), .gameOverW(wonGame), .realGame(gameMode));
gameLimit rounds(.reset, .totalGuesses(totalGuesses), .game(gameMode), .over(lostGame));

// Display options
// Display each guess
guessDisplay G3(.value({SW[7], SW[6]}), .displayOut(guessDisp3));
guessDisplay G2(.value({SW[5], SW[4]}), .displayOut(guessDisp2));
guessDisplay G1(.value({SW[3], SW[2]}), .displayOut(guessDisp1));
guessDisplay G0(.value({SW[1], SW[0]}), .displayOut(guessDisp0));

// Display secret code
guessDisplay Code3(.value(digit3), .displayOut(codeDisp3));
guessDisplay Code2(.value(digit2), .displayOut(codeDisp2));
guessDisplay Code1(.value(digit1), .displayOut(codeDisp1));
guessDisplay Code0(.value(digit0), .displayOut(codeDisp0));

// Display status of game
stateDisplay CL(c.clk(clk[whichClock]), .reset, .in(enterGuess), .value(totalCorrect), .displayOut(locationDisp));
stateDisplay VO(c.clk(clk[whichClock]), .reset, .in(enterGuess), .value(totalValuesOnly), .displayOut(valueDisp));
counter guessesMade(.reset, .in(enterGuess || wonGame), .displayOut10(counter10), .displayOut1(counter1), .guesses(totalGuesses));

// Control displayed game information
always @(*) begin
    if (wonGame && ~lostGame)
        if (SW[8]) begin
            HEX5 = 7'b1111111;
            HEX4 = 7'b1111111;
            HEX3 = codeDisp3;
            HEX2 = codeDisp2;
            HEX1 = codeDisp1;
            HEX0 = codeDisp0;
        end else begin
            HEX5 = 7'b1111111;
            HEX4 = locationDisp;
            HEX3 = 7'b1111111;
            HEX2 = valueDisp;
            HEX1 = counter10;
            HEX0 = counter1;
        end
    else if (lostGame)
        if (SW[8]) begin
            HEX5 = 7'b1111111;
            HEX4 = 7'b1111111;
            HEX3 = codeDisp3;
            HEX2 = codeDisp2;
            HEX1 = codeDisp1;
            HEX0 = codeDisp0;
        end else begin
            HEX5 = 7'b1000111; // L
            HEX4 = 7'b0100011; // O
            HEX3 = 7'b0010010; // S
            HEX2 = 7'b0000110; // E
            HEX1 = 7'b0101111; // R
            HEX0 = 7'b1111111;
        end
    else
        if (SW[8]) begin
            HEX5 = 7'b1111111;
            HEX4 = 7'b1111111;
            HEX3 = guessDisp3;
            HEX2 = guessDisp2;
            HEX1 = guessDisp1;
            HEX0 = guessDisp0;
        end else begin
            HEX5 = 7'b1111111;
            HEX4 = locationDisp;
            HEX3 = 7'b1111111;
            HEX2 = valueDisp;
            HEX1 = counter10;
            HEX0 = counter1;
        end
    end
end
endmodule

```

```

// divided_clocks[0] = 25MHz, [1] = 12.5Mhz, ... [23] = 3Hz, [24] = 1.5Hz, [25] = 0.75Hz, ...
module clock_divider (clock, divided_clocks);
    input logic clock;
    output logic [31:0] divided_clocks;

    initial begin
        divided_clocks <= 0;
    end

    always_ff @(posedge clock) begin
        divided_clocks <= divided_clocks + 1;
    end
endmodule

```

Code 11: DE1_SoC.sv